

CS1050- Lab 3

Index No: 210670N

Name : Vidushini.A.O

Part 1

The assigned task was first to design a circuit for a half adder , then to implement a full adder circuit using half adders using the software Vivado. The second task was to create a symbol for the full adder so that it can be utilized to design new circuits in new projects. The final task was to design a four bit adder circuit using four full adders and simulate the circuit using Xsim


Part 2

- Half Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \text{ XOR } B$$

$$C = A \text{ AND } B$$

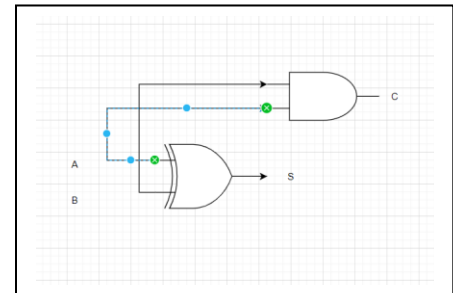

- Full Adder

A	B	C_in	S	C_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Using SoP

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC$$

$$S = \overline{A}(\overline{B}C_{in} + B\overline{C}_{in}) + A(\overline{B}\overline{C}_{in} + BC)$$

$$S = \overline{A}(B \oplus C) + A(\overline{B} \oplus \overline{C})$$

$$S = A \oplus B \oplus C$$


Using SoP

$$C = \overline{A}BC_{in} + A\overline{B}C_{in} + AB\overline{C}_{in} + ABC$$

$$S = \overline{A}(\overline{B}C_{in} + B\overline{C}_{in}) + A(\overline{B}\overline{C}_{in} + BC)$$

$$S = \overline{A}(B \oplus C) + A(\overline{B} \oplus \overline{C})$$

$$S = A \oplus B \oplus C$$

 

Part 3- All VHDL files

HALF ADDER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity HA is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          S : out STD_LOGIC;
          C : out STD_LOGIC);
end HA;

architecture Behavioral of HA is

begin
    S <= A XOR B;
    C <= A AND B;

end Behavioral;

```

FULL ADDER

```

entity FA is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C_in : in STD_LOGIC;
          S : out STD_LOGIC;
          C_out : out STD_LOGIC);
end FA;

architecture Behavioral of FA is
    component HA
    port (
        A1 : in std_logic;
        B1 : in std_logic;
        S1 : out std_logic;
        C1 : out std_logic);
    end component;
    SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : std_logic;
begin
    HA0 : HA
    port map (
        A => A,
        B => B,
        S => HA0_S,
        C => HA0_C);
    HA1 : HA
    port map (
        A => HA0_S,
        B => C_in,
        S => HA1_S,
        C => HA1_C);
    S <= HA1_S;
    C_out <= HA1_C OR HA0_C;

end Behavioral;

```

RCA_4

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 03/17/2023 12:46:24 AM
-- Design Name:
-- Module Name: RCA_4 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity RCA_4 is
```

```
entity RCA_4 is
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          A3 : in STD_LOGIC;
          B0 : in STD_LOGIC;
          B1 : in STD_LOGIC;
          B2 : in STD_LOGIC;
          B3 : in STD_LOGIC;
          C_in : in STD_LOGIC;
          S0 : out STD_LOGIC;
          S1 : out STD_LOGIC;
          S2 : out STD_LOGIC;
          S3 : out STD_LOGIC;
          C_out : out STD_LOGIC);
end RCA_4;


architecture Behavioral of RCA_4 is
    component FA
        port(
            A: in std_logic;
            B: in std_logic;
            C_in: in std_logic;
            S: out std_logic;
            C_out: out std_logic);
        end component;

    SIGNAL FA0_S, FA0_C,FA1_S, FA1_C,FA2_S, FA2_C,FA3_S, FA3_C: std_logic;

begin
    FA_0 :FA
        port map(
            A => A0,
            B=> B0,
            C_in => C_in,
            S => S0,
            C_out => FA0_C
        );
end Behavioral;
```

```

    FA_1 :FA
        port map(
            A => A1,
            B=> B1,
            C_in => FA0_C,
            S => S1,
            C_out => FA1_C
        );
    FA_2 :FA
        port map(
            A => A2,
            B=> B2,
            C_in => FA1_C,
            S => S2,
            C_out => FA2_C
        );
    FA_3 :FA
        port map(
            A => A3,
            B=> B3,
            C_in => FA2_C,
            S => S3,
            C_out => C_out
        );
end Behavioral;
```

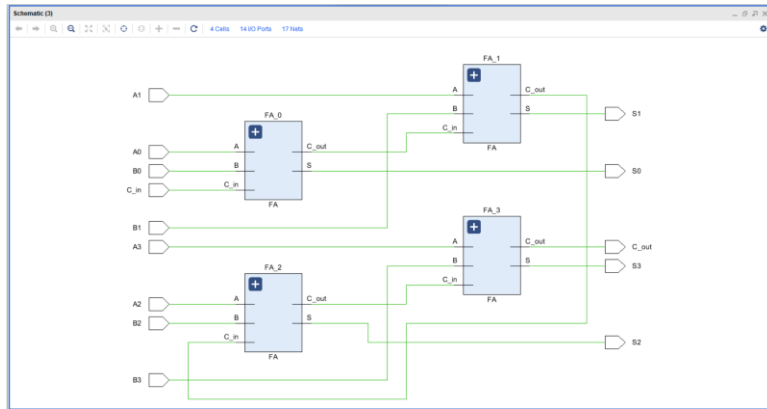


Schematic Diagram of the 4 bit Ripple Adder

Part 4- All Timing Graphs


HALF ADDER



FULL ADDER

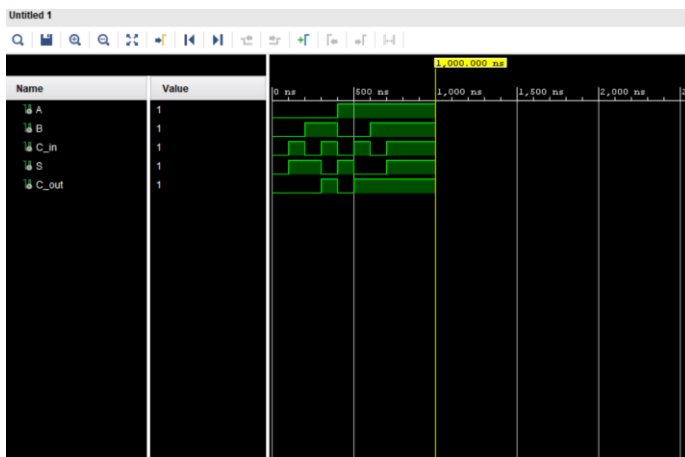

RCA_4

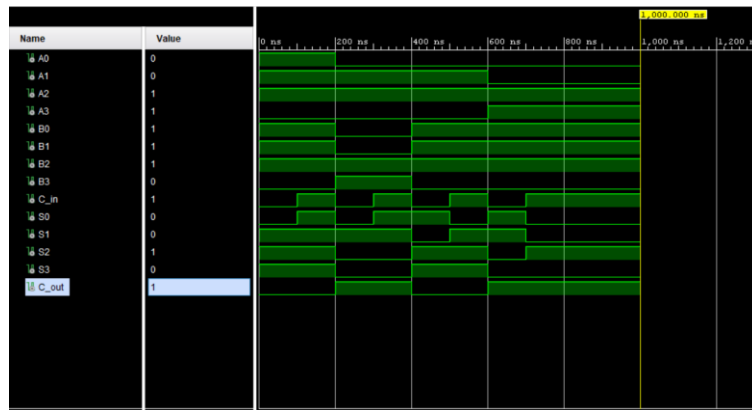

Part 4- why some of the input combinations results in outputs that cannot be represented using LED LD0-LD3. Discuss the role of LD15?

Some of the input combinations results more than 4 bits which is five bits where it cannot be represented using 4 LED s

As an Example:

$$\begin{array}{r} 1111 \\ +1110 \\ \hline 11101 \end{array}$$

In this case the result cannot be represented alone with LED LD0-LD3 , To represent the overhead bit (circled in red in this case), the C_out signal which is represented by LD15 is used.

Part 5 – Other Conclusions

- With the hierarchical design, complex components can be designed using many basic components.
- A macro symbol can be built (Block) of a certain component to make it able to used in future designs in other Vivado projects.
- A full adder can be designed using two half adders and even more complex bit adders like the 4 bit ripple adder can be designed out of several full adder circuits.